

INTERFACING PIC MICROCONTROLLERS

Embedded Design by Interactive Simulation

Martin Bates

CONTENTS

Preface

Introduction

Links, References & Acknowledgements

PART 1 PIC MICROCONTROLLER

Chapter 1 PIC HARDWARE

Summary 1

1.1 Processor System

1.1.1 Processor

Figure 1.1 Block diagram of a basic micro system

1.1.2 Memory

Figure 1.2 Microprocessor program execution

1.1.3 Input and Output

Table 1.1 Memory and data storage technologies

Figure 1.3 Parallel and serial data

1.2 PIC Architecture

1.2.1 PIC 16F877A Pin Out

Figure 1.4 PIC 16F877A pin out

1.2.2 PIC 16F877A Architecture

Figure 1.5 Program execution block diagram

1.2.3 The PIC Instruction

Table 1.2 16F877A File register set

1.3 Special Function Registers

1.3.1 Program Counter

1.3.2 Status Register

Table 1.3 Status register bits

Table 1.4 Arithmetic results

Table 1.5 Register bank select

1.3.3 Ports

Table 1.6 Port alternate functions

- 1.3.4 Timers
- 1.3.5 Indirect Addressing
- 1.3.6 Interrupt Control
- 1.3.7 Peripheral Control

Table 1.7 Typical configurations for Timer 0

Table 1.8 Interrupt sources and control bits

1.4 Application LED1

- 1.4.1 LED1 Hardware
- 1.4.2 Simple PIC Program
- 1.4.3 Writing the Program
- 1.4.4 Simulation of LED1

Figure 1.6 LED1 schematic

Program 1.1 LED1 List File

Figure 1.7 MPLAB8 screenshot of LED1

Table 1.9 Quickbuild fileset

1.5 Program Downloading

- 1.5.1 ICPD
- 1.5.2 ICPD hardware
- 1.5.3 LED1 testing
- 1.5.4 Development steps

Figure 1.8 PIC programming methods

Figure 1.9 ICPD programming connections

Figure 1.10 ICD3 & RealICE pic

Figure 1.11 16F877A test rig

1.6 Conversion to 16F887

Figure 1.12 16F887 pin out

Questions 1

Assignments 1

Chapter 2 PIC PROGRAMMING

Summary 2

2.1 Application LED2

Figure 2.1 LED2 Hardware Outline

Program 2.1 LED2 List File

Figure 2.2 LED2 simulation in MPLABX

2.2 Assembly Language

- 2.2.1 Assembler Code
- 2.2.2 Assembler Syntax

Table 2.1 List File Elements

Table 2.2 Instruction analysis

2.3 MCU Configuration

- 2.3.1 PROCESSOR Directive
- 2.3.2 CONFIG directive
- 2.3.3 Typical MCU configurations

Table 2.3 Configuration bits

2.4 PIC Instruction Set

Table 2.4 PIC instruction

- 2.4.1 Instruction Types
- 2.4.2 Obsolete Instructions

2.5 Program Execution

- 2.5.1 Subroutines
- 2.5.2 Page Boundaries
- 2.5.3 Interrupts

Figure 2.3 Program memory and stack

2.6 Program Structure

2.7 Assembler Directives

Program 2.2 LED3 list file with assembler directives

- 2.7.1 Common Directives
- 2.7.2 Macros
- 2.7.3 LED3 List File

Table 2.5 Selected assembler directives

2.8 Software Design

- 2.8.1 Application Specification
- 2.8.2 Flowcharts
- 2.8.3 Pseudocode
- 2.8.4 Structure charts

Figure 2.4 LED2 Flowcharts

Table 2.6 Flowchart implementation

Figure 2.5 LED2 outline

Figure 2.6 LED2 Structure Chart

2.9 'C' Programming

- 2.9.1 LEDC Program
- 2.9.2 LEDC Assembler Code
- 2.9.3 Real Time OS

Program 2.3 LED4 C Source Code

Program 2.4 LED4 list file

Questions 2

Assignments 2

Summary 3

3.1 Circuit Design

- 3.1.1 Drawing the schematic
- 3.1.2 Circuit simulation
- 3.1.3 Setting up the simulation
- 3.1.4 Running the simulation

Figure 3.1 LED2 Hardware schematic

Figure 3.2 ISIS screenshot

Figure 3.3 Picking a device

Figure 3.4 MCU properties

Figure 3.5 Source code debugging

3.2 Software Debugging

- 3.2.1 Source Debug Window
- 3.2.2 CPU Register Window
- 3.2.3 Data Memory
- 3.2.4 Watch Window

Figure 3.6 Source debug menu

3.3 Virtual Testing

- 3.3.1 Probes & Meters
- 3.3.2 Timer/Counter
- 3.3.3 Oscilloscope
- 3.3.4 Logic Analyser
- 3.3.5 Graphs

Figure 3.7 Voltmeter and ammeter

Figure 3.8 Test instruments

Figure 3.9 Oscilloscope display

Figure 3.10 Logic analyser display

3.4 Hardware Design

- 3.4.1 Netlist
- 3.4.2 PCB Layout

Figure 3.11 LED2 Netlist

Figure 3.12 PCB Layout

3.5 Hardware Testing

- 3.5.1 ICPD requirements
- 3.5.2 ICPD testing
- 3.5.3 16F877A Electrical Characteristics

Questions 3

Assignments 3

PART2 PIC INTERFACING

Chapter 4 INPUT & OUTPUT

Summary 4

4.1 Switched Inputs

- 4.1.1 Switch interface
- 4.1.2 Supply voltage
- 4.1.3 Hardware Switch Debouncing
- 4.1.4 Software Switch Debouncing
- 4.1.5 Timer Switch Debouncing

- 4.1.6 Switch Input Interrupts

Figure 4.1 Prototype target board

Figure 4.2 Switch photos and circuit

Figure 4.3 Switch bounce

Program 4.1 COUNT1 Software debounce

Program 4.2 COUNT2 timer debounce

Figure 4.4 Timer 0 block diagram

Program 4.3 COUNT3 Interrupts

4.2 Display Outputs

- 4.2.1 LED Output Circuit
- 4.2.2 LED Opto-isolator
- 4.2.3 7-Segment LED Display

Figure 4.5 LED based components

Figure 4.6 LED opto-isolator

Table 4.1 7-Segment codes

4.3 Keypad System

- 4.3.1 Keypad interface
- 4.3.2 Keypad program
- 4.1.3 Keyboards

Figure 4.7 Keypad connections & circuit

Program 4.4 KEYPAD2 source code

4.4 Liquid Crystal Display

- 4.4.1 LM016L LCD application

- 4.4.2 LCD demo program

- 4.4.3 ASCII codes
- 4.2.5 LCD display modes

Figure 4.8 LCD demo board photo

Figure 4.9 LCD display schematic

Table 4.2 LCD Command set

Program 4.5 LCD2 source code

Figure 4.10 LCD program outline

Figure 4.11 LCD block diagram

Questions 4

Assignments 4

Chapter 5 DATA PROCESSING

Summary 5

5.1 Number Systems

- 5.1.1 Denary
- 5.1.2 Binary
- 5.1.3 Hexadecimal
- 5.1.4 Other number systems

Table 5.1 Structure of a denary number

Table 5.2 Structure of a binary number

Table 5.3 Structure of a hex number

5.2 Numerical Conversion

- 5.2.1 Binary to decimal
- 5.2.2 Decimal to binary
- 5.2.3 Binary and Hex

5.3 Binary Arithmetic

- 5.3.1 Addition
- 5.3.2 Subtraction
- 5.3.3 Multiplication
- 5.3.4 Division

5.4 Numerical Types

- 5.4.1 Positive Integers
- 5.4.2 Negative Integers
- 5.4.3 2s Complement Arithmetic
- 5.4.4 2s Complement Conversion
- 5.4.5 Floating Point Numbers

Table 5.4 Numerical types

Table 5.5 Structure of FP number

5.5 BCD and ASCII

- 5.5.1 BCD Calculations
- 5.5.2 BCD to Binary Conversion
- 5.5.3 Characters and strings

Table 5.6 BCD Calculations

Figure 5.1 BCD add process

Figure 5.2 BCD to binary process

Table 5.7 ASCII Character Set

5.6 Calculator Application

- 5.6.1 Calculator Hardware
- 5.6.2 Calculator Program

Figure 5.3 Calculator schematic

Figure 5.4 Calculator program outline

Program 5.1 Calculator source code

5.7 Data Storage

- 5.7.1 Memory System Hardware
- 5.7.2 Memory Test Program
- 5.7.3 Extended Memory System

Figure 5.5 Parallel memory system

Program 5.2 Memory test source code

Figure 5.6 Extended memory system

Questions 5

Assignments 5

Chapter 6 ANALOGUE INTERFACING

Summary 6

6.1 Analogue Input

- 6.1.1 8-bit test circuit
- 6.1.2 ADC operation
- 6.1.3 ADC clock
- 6.1.4 Results registers
- 6.1.5 8-bit program
- 6.1.6 10-bit ADC input

Figure 6.1 Stepwise ADC

Figure 6.2 8-bit ADC schematic

Figure 6.3 ADC block diagram

Figure 6.4 ADC test program outline

Program 6.1 8-bit analogue input test program

Figure 6.5 10-bit conversion circuit

Figure 6.6 10-bit BCD routine outline

Program 6.2 10-bit conversion

6.2 Op-amp Interfaces

- 6.2.1 Ideal Amplifier
- 6.2.2 Basic configurations
- 6.2.3 Non-inverting Amplifier
- 6.2.4 Inverting Amplifier
- 6.2.5 Unity Gain Buffer
- 6.2.6 Summing Amplifier
- 6.2.7 Difference Amplifier
- 6.2.8 Universal Amplifier

Figure 6.7 Op-amp equivalent circuit

Figure 6.8 Basic amplifier configurations

Figure 6.9 Opamp test circuits

Table 6.1 Opamp Test results

Figure 6.10 Universal amplifier

6.3 Circuit Design

- 6.3.1 Component values
- 6.3.2 Voltage divider
- 6.3.3 Gain & Offset
- 6.3.4 Amplifier Calibration

Figure 6.11 Voltage divider

Figure 6.12 Gain & offset circuit

- 6.3.5 Input resistance *Figure 6.13 Input resistance*
- 6.3.6 Input capacitance *Figure 6.14 RC network*
- 6.3.7 Transient response *Figure 6.15 Feedback capacitance*

6.4 Frequency Response

- 6.4.1 Low pass filter *Figure 6.16 Low pass frequency response*
- 6.4.2 Internal compensation
- 6.4.3 Gain/bandwidth product *Figure 6.17 Gain/bandwidth product*
- 6.4.4 AC coupling *Figure 6.18 Audio amp FR*
- 6.4.5 Band pass amplifier

6.5 Op-amp Selection

- 6.5.1 Op-amp types
- 6.5.2 Op-amp supplies
- 6.5.3 Op-amp characteristics

Table 6.2 Op-amp comparison

6.6 Comparators

- 6.6.1 Simple comparator
- 6.6.2 Trigger comparator
- 6.6.3 Window comparator

Figure 6.19 Comparators

6.7 Op-amp applications

- 6.7.1 Instrumentation amplifier *Figure 6.20 Instrumentation Amplifier*
- 6.7.2 Current Loop *Figure 6.21 Constant current source*
Figure 6.22 Current loop system
- 6.7.3 Logarithmic amplifier *Figure 6.23 Diode clamp*
Figure 6.24 Log amp

6.8 AC Signal Measurement

- 6.8.1 Peak Detector *Figure 6.25 Peak detector simulation*
- 6.8.2 Frequency Measurement *Figure 6.26 Frequency measurement block*
- 6.8.3 Digital Sampling *Figure 6.27 Principles of digital sampling*

6.10 Analogue Output

- 6.9.1 DAC Types *Figure 6.28 DAC operation*
- 6.9.2 Parallel DAC *Figure 6.29 DACS test circuit schematic*
- 6.9.3 Serial DAC
- 6.9.4 DAC program *Program 6.3 DACS test program*

Questions 6

Assignments 6

Chapter 7 POWER OUTPUTS

Summary 7

7.1 Power Loads

7.1.1 Relay

Figure 7.1 Electromagnetic devices

7.2.2 DC Motor

7.3.3 Real Motors

7.2 Power Interfaces

Figure 7.2 Power output circuits

7.2.1 Relay Interface

7.2.2 Thyristor & Triac

Figure 7.3 Thyristor and Triac

7.2.3 Oscillator Interface

7.3 Current Switches

7.3.1 Bipolar transistor

Figure 7.4 Bipolar transistor

7.3.2 FET switches

Figure 7.5 Transistor switch circuits

7.4 Pulse Applications

7.4.1 Pulse output

Figure 7.6 Pulse Output Simulation

Figure 7.7 Timer 1 Compare mode

Figure 7.8 Pulse Output Program Outline

Program 7.1 Pulse Output

7.4.2 PWM output

Figure 7.9 PWM mode registers

7.4.3 Pulse input

Figure 7.10 Input Timing Simulation

Figure 7.11 Capture Mode Block & Registers

Figure 7.12 Input Period Program Outline

Program 7.2 Input Period Measurement

7.5 DC Motor

7.5.1 Bipolar drive

Figure 7.13 Motor bridge drives

7.5.2 FET bridge

Figure 7.14 Motor interfaces schematic

7.5.3 Test circuit

Figure 7.15 Motor Test Program Outline

7.5.4 PWM drive

Program 7.3 Motor Test Program

7.6 Stepper Motor

Figure 7.16 Stepper Motor Operation

7.7 BLDC Motor

Figure 7.17 Remote control helicopter

Figure 7.18 BLDC motor control schematic

Program 7.4 BLDC source code

7.8 Mechatronics Board

Figure 7.19 PIC mechatronics board photo

Figure 7.20 PIC mechatronics board schematic

Table 7.1 Half-bridge control logic

7.9 Servo Systems

7.9.1 Digital feedback

Figure 7.21 Servo systems

7.9.2 Servo control

7.9.3 Digital servo

7.9.4 Analogue servo

7.9.5 Hobby Servo

Figure 7.22 Hobby servo photo & signal

Questions 7

Assignments 7

PART 3 PIC SYSTEMS

Chapter 8 SERIAL COMMUNICATION

Summary 8

8.1 USART

- 8.1.1 RS-232 *Figure 8.1 USART connections & signal*
- 8.1.2 Test System *Figure 8.2 USART simulation*
Figure 8.3 USART program outline
Program 8.1 USART demo program

8.2 SPI Bus

- Figure 8.4 SPI Operation*
- Figure 8.5 SPI Test Circuit*
- Program 8.2 SPI Master & Slave Programs*

8.3 I²C Bus

- Figure 8.6 I2C Operation*
- Figure 8.7 I2C System Simulation*
- 8.3.1 Signal format *Table 8.1 I2C Data Format*
- 8.3.2 Transmission control *Figure 8.8 I2C Program Outline*
Program 8.3 I2C Memory Test
Table 8.2 I2C Registers

8.4 Network Links

- 8.4.1 CAN Bus *Figure 8.9 CAN bus*
- 8.4.2 LIN Bus *Figure 8.10 LIN bus*
- 8.4.3 USB
- 8.4.4 Synchronous data *Figure 8.11 Sync encoding*
- 8.4.5 Ethernet

8.5 Wireless Links

- 8.5.5 Infrared *Figure 8.12 IR interface block and signals*
- 8.5.6 Radio Links
- 8.5.7 Wi-Fi
- 8.5.8 Zigbee *Figure 8.13 Zigbee transceiver photo*

8.6 Comparison of serial links

Table 8.3 Comparison of serial links

Questions 8

Assignments 8

Chapter 9 INPUT SENSORS

Summary 9

9.1 Digital Sensing

Figure 9.1 Sensor photos

9.1.1 Mechanical

9.1.2 Opto-switch

Figure 9.2 Opto-detector

9.1.3 Opto-encoder

Figure 9.3 Opto encoding

9.2 Analogue Sensing

Figure 9.4 Sensor characteristics

9.2.1 Sensitivity

9.2.2 Offset

9.2.3 Transfer function

Figure 9.5 Linear temp sensor graph

9.2.4 Linearity

9.2.5 Other error factors

9.2.6 Response time

9.3 Position Sensors

Table 9.1 Position Sensors

9.3.1 Switched

9.3.2 Resistive

9.3.3 Capacitive

9.3.4 Inductive

9.3.5 Ultrasonic

9.4 Temperature Sensing

Table 9.2 Temperature sensors

9.4.1 Metallic

9.4.2 Thermocouple

9.4.3 Thermistor

9.4.4 Interface

Figure 9.6 Resistive sensor interface

9.5 Semiconductor Sensors

- 9.5.1 Semiconductor Junction *Figure 9.7 Diode temp sensor*
- 9.5.2 Temperature Sensitivity
- 9.5.3 Diode Sensor
- 9.5.4 Integrated Temperature Sensor *Figure 9.8 LM35 interface*

9.6 Light Sensors

Table 9.3 Light, Force, Humidity

- 9.6.1 Photodiode
- 9.6.2 Phototransistor
- 9.6.3 Light Dependent Resistor
- 9.6.4 Integrated Light Sensor

Figure 9.9 LDR plot & photo

9.7 Force Sensors

- 9.7.1 Strain Gauge
- 9.7.2 Pressure Sensor

Figure 9.10 Strain gauge circuit

9.8 Humidity Sensors

Figure 9.11 Humidity interface

9.9 IC Sensors

Figure 9.12 IC sensors schematic

- 9.9.1 Distance
- 9.9.2 Pressure
- 9.9.3 Humidity and Temperature

Questions 9

Assignments 9

Chapter 10 SYSTEM DESIGN

Summary 10

10.1 PIC MCU Selection

Table 10.1 8-bit PIC families

- 10.1.1 Compact 8-bit PICs
- 10.1.2 Mid-range 8-bit PICs
- 10.1.3 Power 8-bit PICs

Table 10.2 Selected 8-bit PICs

10.2 Power Supplies

- 10.2.1 Mains supplies

- 10.2.2 Battery supplies
- 10.2.3 PIC supplies
- 10.2.4 System supplies

10.3 System Design

- 10.3.1 Specification *Figure 10.1 Block diagram of refrigeration controller*
- 10.3.2 Design Outline *Figure 10.2 Refrigeration control system*
- 10.3.3 Implementation *Figure 10.3 Refrigeration controller program outline*

10.4 BASE System

- Figure 10.4 Base module block diagram*
- 10.4.1 BASE board hardware *Figure 10.5 Base module schematic*
- 10.4.2 BASE board test program *Program 10.1 Base module test program*

10.5 Weather Station

- Table 10.3 Weather Station Specification*
- Figure 10.6 Block Diagram of Weather Station*
- 10.5.1 Temperature Sensor Interface *Figure 10.7 Temperature Sensor Interface*
- 10.5.2 Light Sensor Interface *Figure 10.8 Light Sensor Interface*
- 10.5.3 Humidity Sensor Interface *Figure 10.9 Humidity Sensor Interface*
- 10.5.4 Pressure Sensor Interface *Figure 10.10 Pressure Sensor Interface*

10.6 Design Support

Questions 10

Assignments 10

Appendix A PIC 16F(L)877A Electrical Characteristics

Appendix B Digital Signal Transmission

Index